

# SINGLE PHASE FULL BRIDGE INVERTER (HARDWARE APPROACH)
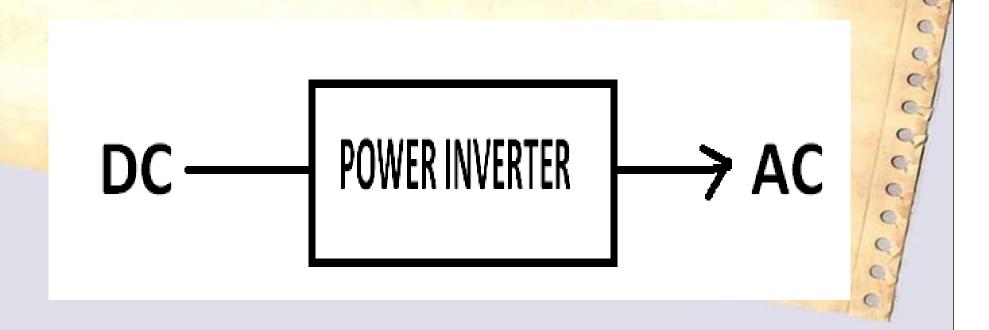
#### What is INVERTER?

A POWER INVERTER IS AN ELECTRICAL DEVICE THAT CHANGES DIRECT CURRENT (DC) TO ALTERNATING CURRENT (AC).



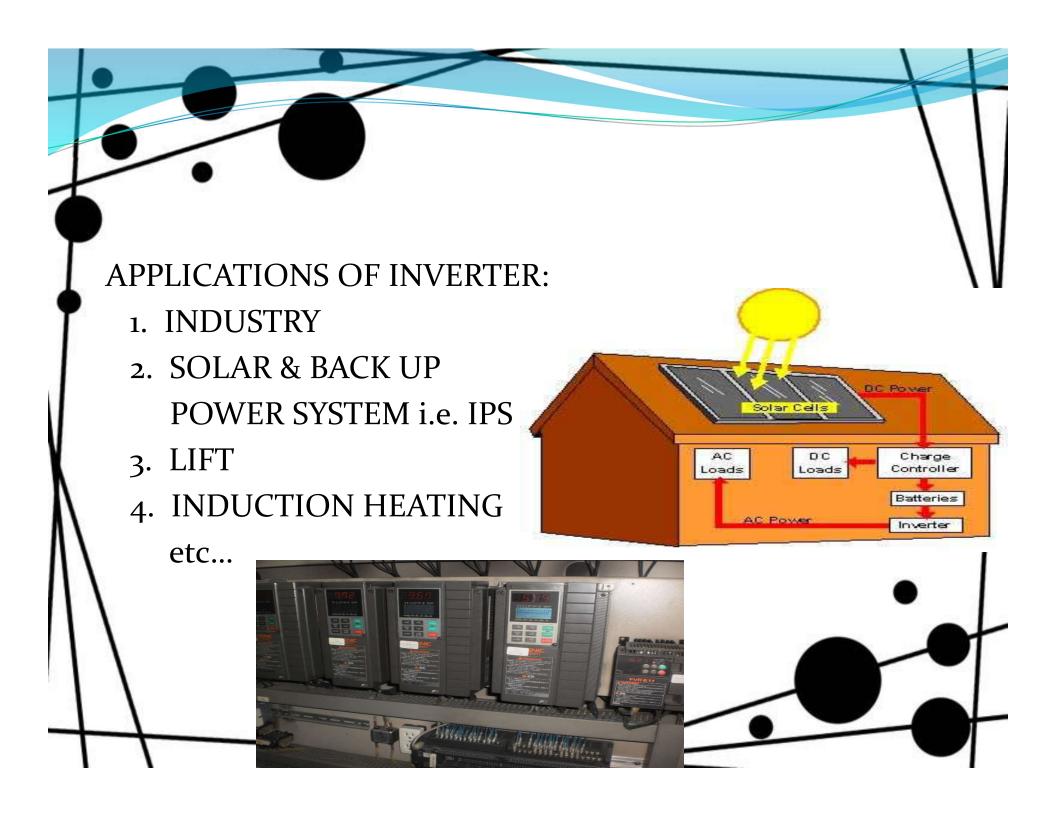

#### There are Three kind of INVERTER


- 1.PUSH PULL INVERTER
- 2.HALF BRIDGE INVERTER
- 3.FULL BRIDGE INVERTER
- THERE MORE EFFICIENCY INVERTER IS FULL BRIDGE INVERTER(50%)
- FULL BRIDGE INVERTER




## **BLOCK DIAGRAM OF OUR INVERTER DC POWER OUTPUT SUPPLY AC VOLTAGE ACROSS THE LOAD 4 SEMICONDUCTOR SWITCHES** (MOSFETS -Q1,Q2,Q3,Q4) **OPTOCOUPLER OPTOCOUPLER SIGNAL GENERATOR** Q1 & Q4 Q2 & Q3

#### 666666666666666666666666666666666

#### CIRCUIT DETAILS

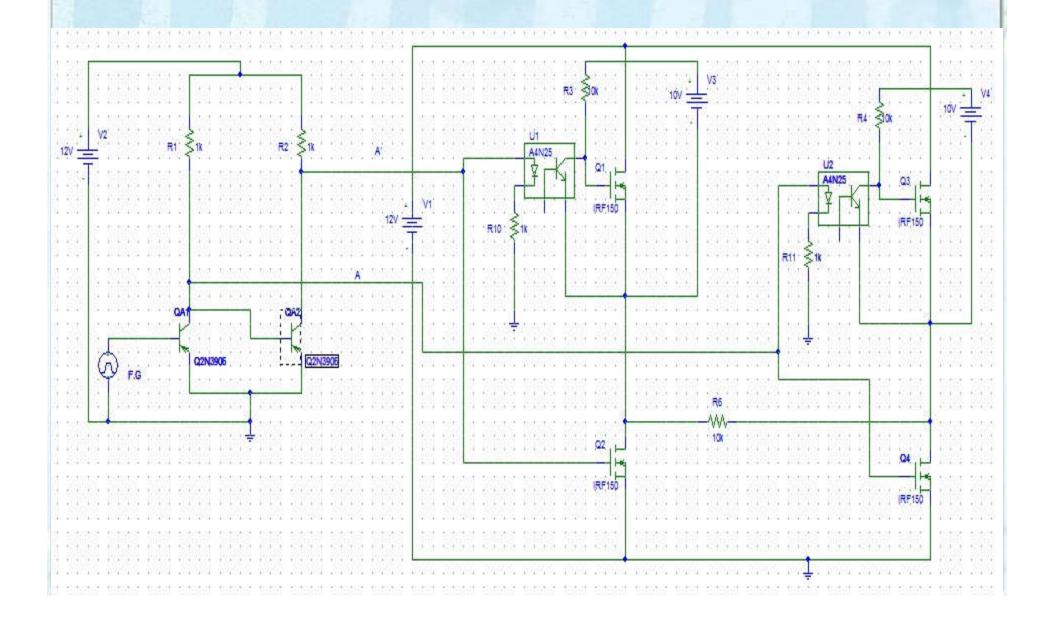

# EXPERIMENTAL SET UP

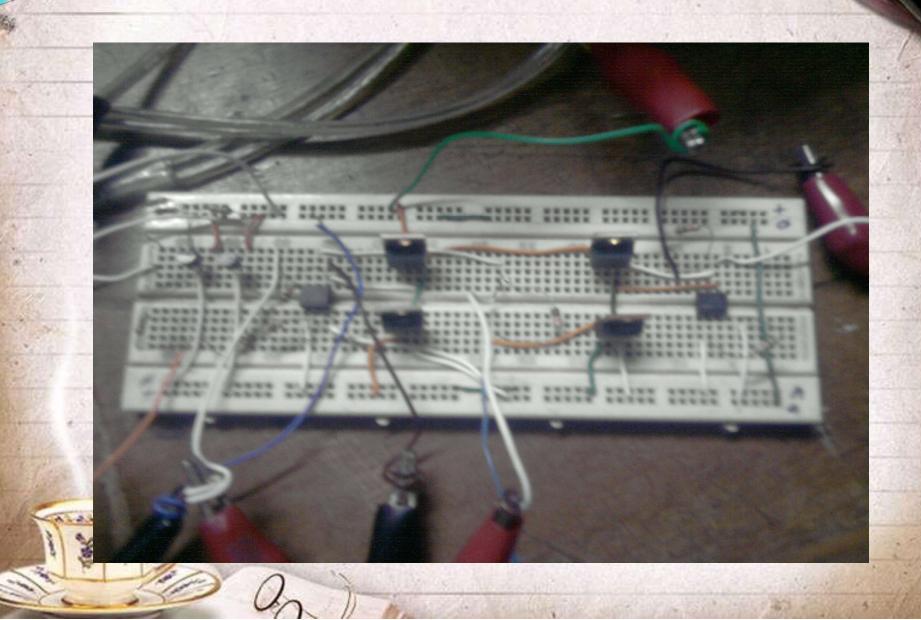

# **OBSERVATIONS**







## **OUTPUT CALCULATIONS**

CASE1: Vs=12V,  $R_{L}=1K\Omega$ ,  $I_{L}=0.012A$ , P=0.144W

CASE2: Vs=15V,  $Rl=1K\Omega$ , Il=0.015 A P=0.225W



#### FEATURES OF OUR INVERTER

- 1. HIGH EFFICIENCY
- 2. SIMPLE CIRCUITRY TO MAINTENANCE
- 3. HIGH POWER HANDLING CAPABILITY

#### If use in IPS FULL BRIDGE INVERTER

• In our Bangladesh all IPS company use push pull inverter.....(20~25)%

• If we use full bridge inverter than.....we get EFFICIENCY more than 50%

• So our energy are save.....

